## **Year 5/6 Electricity Knowledge Organiser**












#### What do I know?

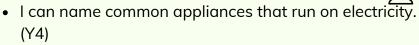

- I know that some appliances use mains electricity, some use batteries and some use both. (Y4)
- I can construct a simple circuit including cells, wires, bulbs, switches and buzzers. (Y4)
- I can identify a complete and incomplete circuit. (Y4)
- I know that a switch can open and close a circuit. (Y4)
- I can name some conductors and insulators. I know metal is a good conductor. (Y4)

## Gems of knowledge

- I will investigate how to increase the brightness of a bulb or the volume of a buzzer.
- I will construct a simple series circuit.
- I will use a switch to turn a circuit on or off.
- I will use circuit symbols to draw simple circuit diagrams.

#### How will I work like a Scientist?



Plan different types of scientific enquiries to answer a variety of scientific questions.

Recognise and control variables where necessary (Y5- with support).






Meaning

Circuit



A complete path that an electrical current can flow around.

Circuit diagram

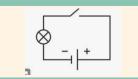


Scientific drawing of a circuit using symbols.

Component



A part of an electrical circuit.

Cell/battery

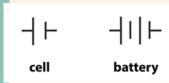

A device that stores energy until it is needed. A cell is single unit. A battery is a collection of cells.

Voltage




The force that makes the electric current move through the wires

Current



The flow of electric charge in a circuit.

### Significant Scientist

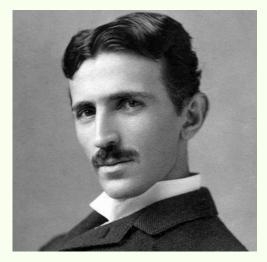

Nikola Tesla was a successful inventor and engineer. He is best known for his part in the design of the modern alternating current (AC) electricity supply system. Tesla Motors was named after him.

**Q** Careers in Physics (Electricity)

A electrical engineer fixes and designs new and better ways of using devices that use electricity.

X

# Read me!



The Boy Who Invented TV by Kathleen Krull and Greg Couch

The Lighthouse Keeper's Lunch by Ronda and David Armitage.

